

# BJT Transistor Modeling

Rabiul Al Mahmud

Lecturer, EEE, IUT




Department of Electrical and Electronic Engineering,  
Islamic University of Technology (IUT).

## BJT Transistor Modeling

- A model is a combination of circuit elements, properly chosen, that best approximates the actual behavior of a semiconductor device under specific operating conditions.
- Once the ac equivalent circuit is determined, the schematic symbol for the device can be replaced by this equivalent circuit and the basic methods of circuit analysis applied to determine the desired quantities of the network.
- There are two models commonly used in small signal AC analysis of a transistor:
  - $r_e$  model
  - Hybrid equivalent model


## BJT Transistor Modeling

The dc levels were simply important for determining the proper Q-point of operation. Once determined, the dc levels can be ignored in the ac analysis of the network. In addition, the coupling capacitors  $C_1$  and  $C_2$  and bypass capacitor  $C_3$  were chosen to have a very small reactance at the frequency of application.

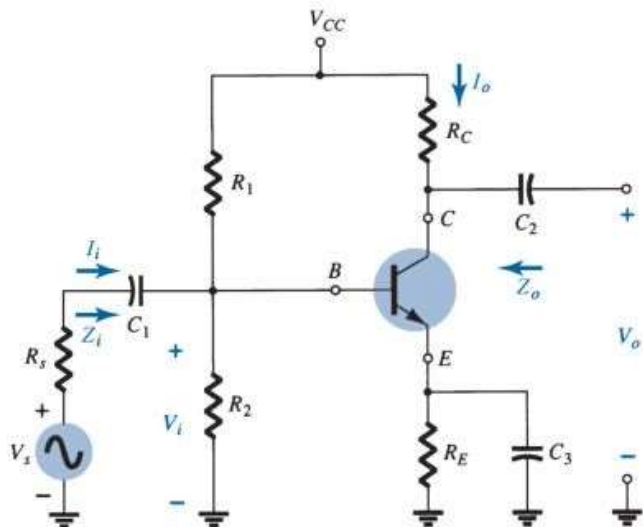

**FIG. 3**

Transistor circuit under examination in this introductory discussion.

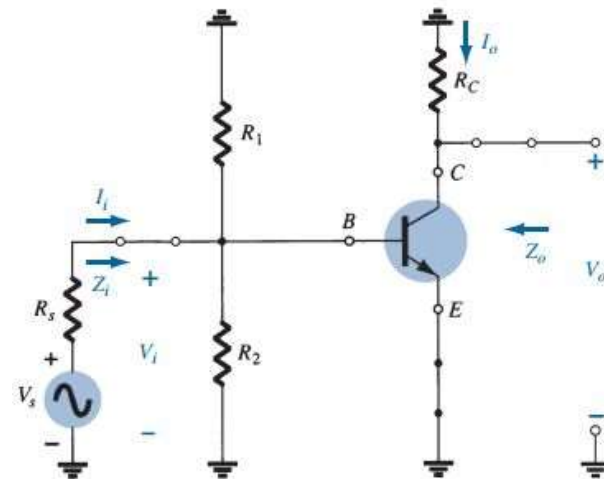


**FIG. 4**

The network of Fig. 3 following removal of the dc supply and insertion of the short-circuit equivalent for the capacitors.

## BJT Transistor Modeling

- Setting all dc sources to zero and replacing them by a short-circuit equivalent
- Replacing all capacitors by a short-circuit equivalent
- Removing all elements bypassed by the short-circuit equivalents introduced by steps 1 and 2
- Redrawing the network in a more convenient and logical form

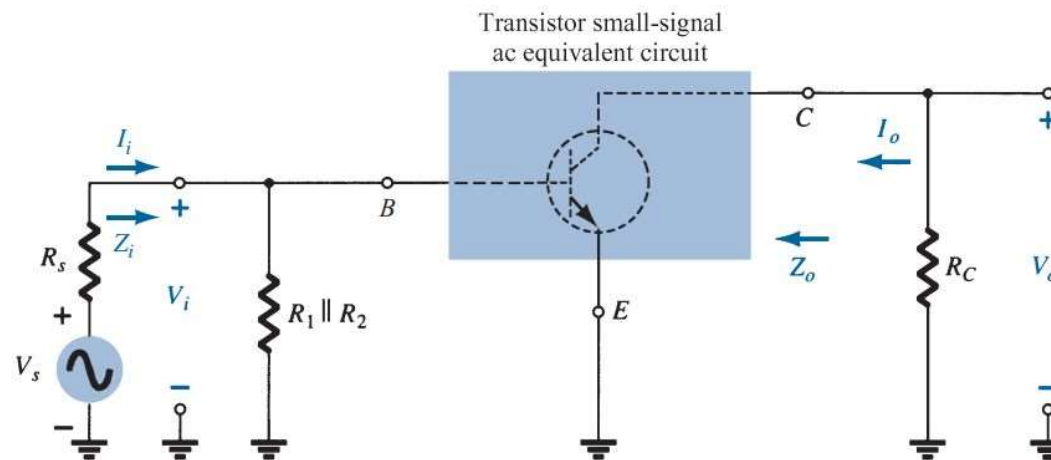


**FIG. 7**

*Circuit of Fig. 4 redrawn for small-signal ac analysis.*


## BJT Transistor Modeling

- Voltage Gain
- Current Gain

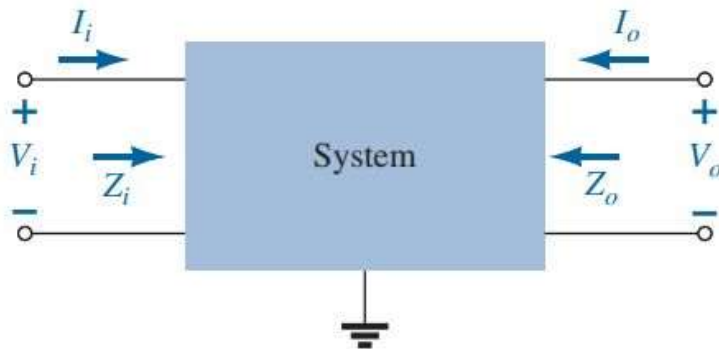

**FIG. 5**

*Defining the important parameters of any system.*

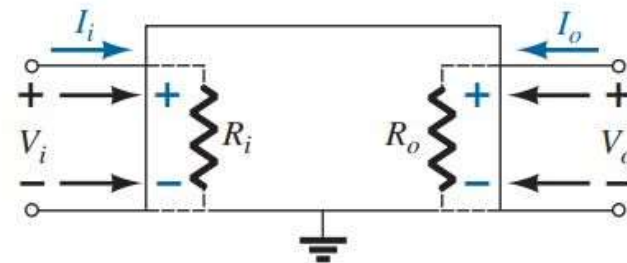


**FIG. 6**

*Demonstrating the reason for the defined directions and polarities.*


## r<sub>e</sub> Model

- Input Equivalent Circuit

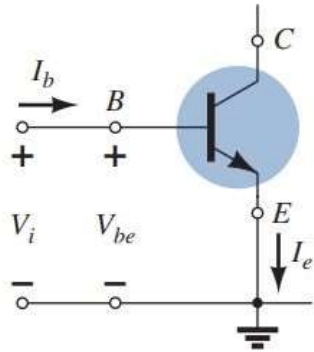


**FIG. 8**

*Finding the input equivalent circuit for a BJT transistor.*

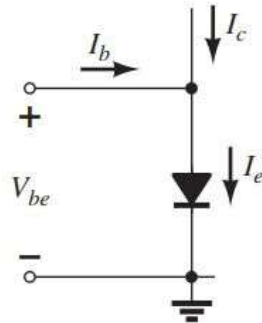

**FIG. 10**

*Equivalent circuit for the input side of a BJT transistor.*

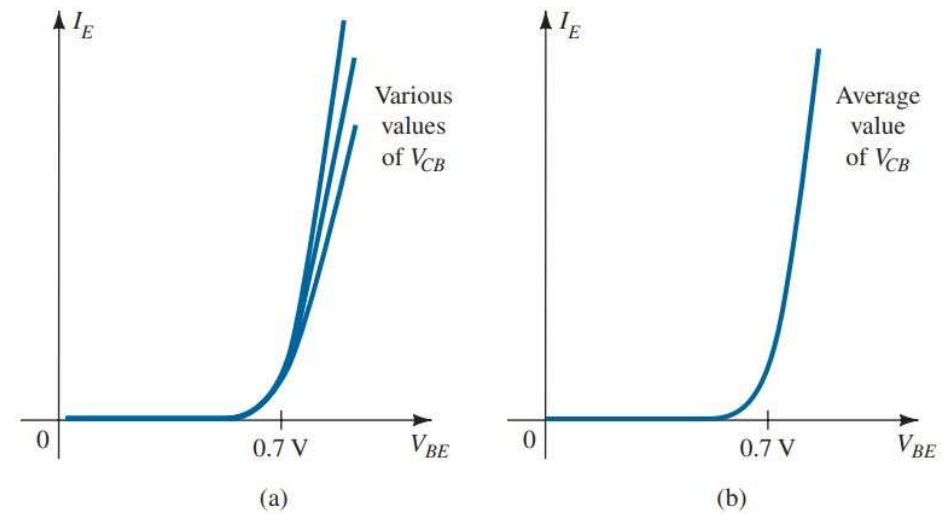


**FIG. 9**

*Defining the average curve for the characteristics of Fig. 9a.*


## r<sub>e</sub> Model

- Equivalent Circuit


It can be improved by first replacing the diode by its equivalent resistance as determined by the level of  $I_E$ .

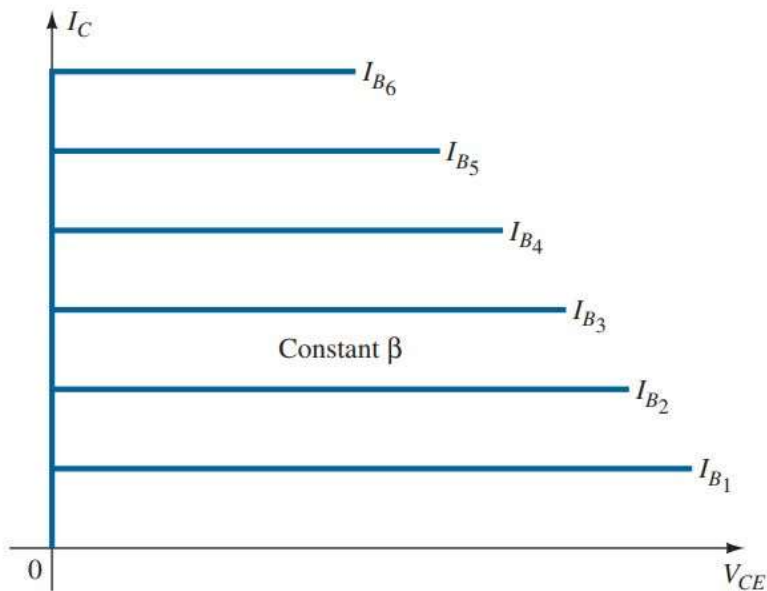

**FIG. 11**  
Constant  $\beta$  characteristics.

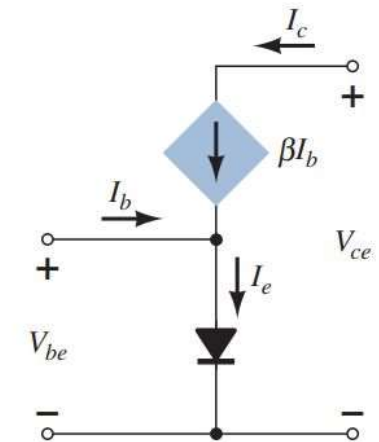


**FIG. 12**  
BJT equivalent circuit.

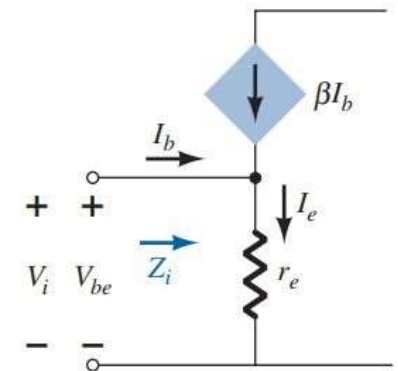

**FIG. 13**  
Defining the level of  $Z_i$ .

## $r_e$ Model

- Equivalent Circuit

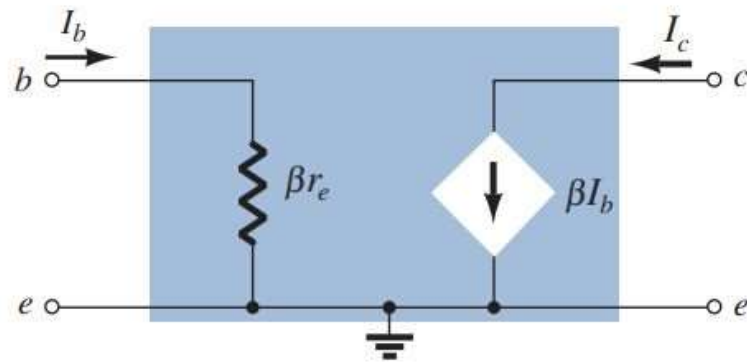


**FIG. 14**

*Improved BJT equivalent circuit.*




## Early Voltage

$$r_o = \frac{\Delta V}{\Delta I} = \frac{V_A + V_{CEQ}}{I_{CQ}}$$

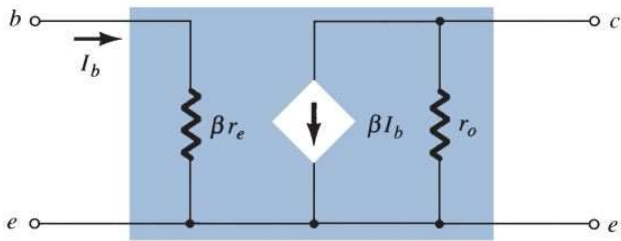

**FIG. 16**


*r<sub>e</sub> model for the common-emitter transistor configuration including effects of r<sub>o</sub>.*

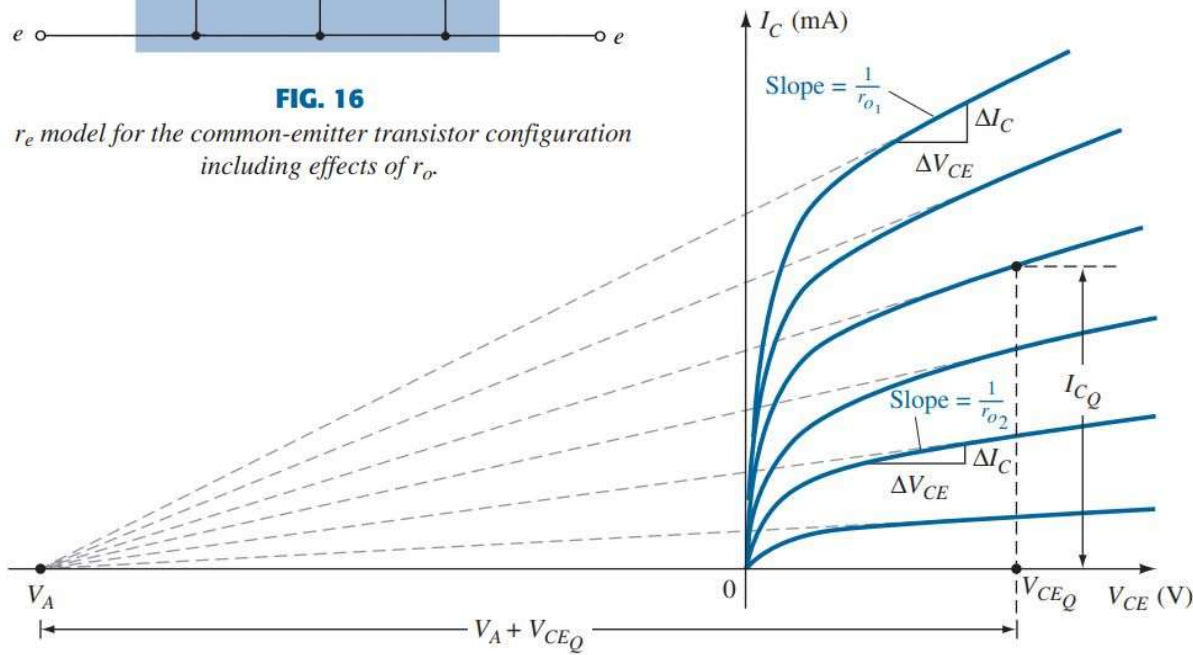

**FIG. 15**


*Defining the Early voltage and the output impedance of a transistor.*

## Common-emitter fixed-bias Configuration

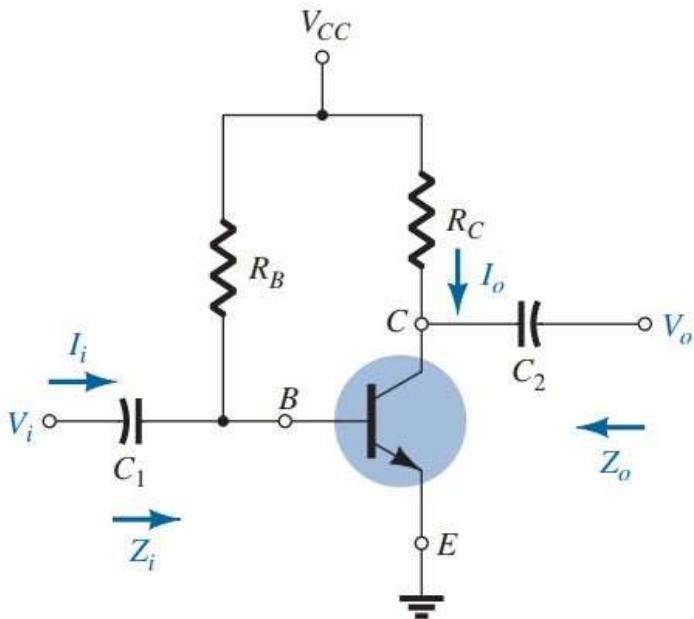

**FIG. 20**


*Common-emitter fixed-bias configuration.*

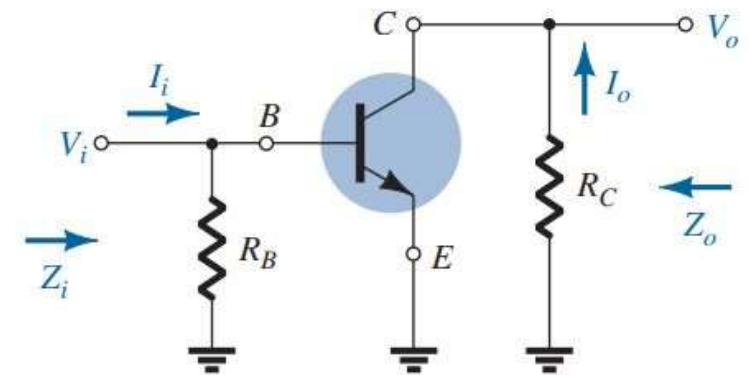

**FIG. 21**


*Network of Fig. 20 following the removal of the effects of  $V_{CC}$ ,  $C_1$ , and  $C_2$ .*

## Common-emitter fixed-bias Configuration

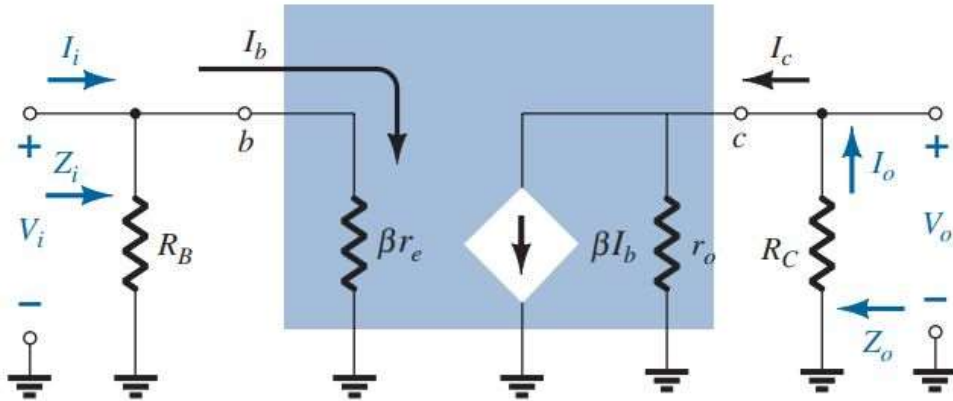

**FIG. 22**


*Substituting the  $r_e$  model into the network of Fig. 21.*

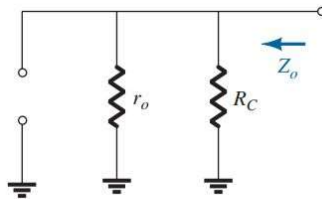

**FIG. 23**

*Determining  $Z_o$  for the network of Fig. 22.*

## Common-emitter fixed-bias Configuration

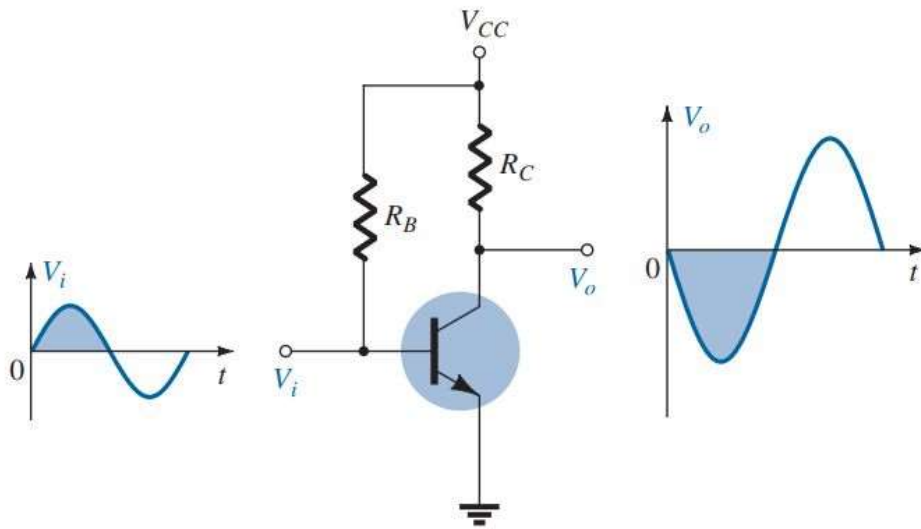


**FIG. 24**

*Demonstrating the  $180^\circ$  phase shift between input and output waveforms.*

## Common-emitter fixed-bias Configuration


**EXAMPLE 1** For the network of Fig. 25:

- Determine  $r_e$ .
- Find  $Z_i$  (with  $r_o = \infty \Omega$ ).
- Calculate  $Z_o$  (with  $r_o = \infty \Omega$ ).
- Determine  $A_v$  (with  $r_o = \infty \Omega$ ).
- Repeat parts (c) and (d) including  $r_o = 50 \text{ k}\Omega$  in all calculations and compare results.

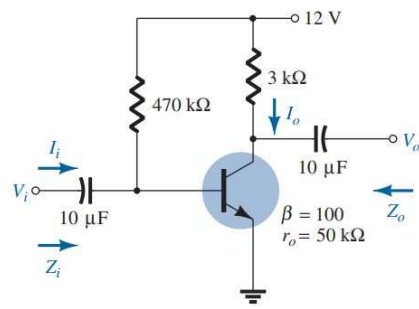


**FIG. 25**  
Example 1.

## Voltage-divider Bias

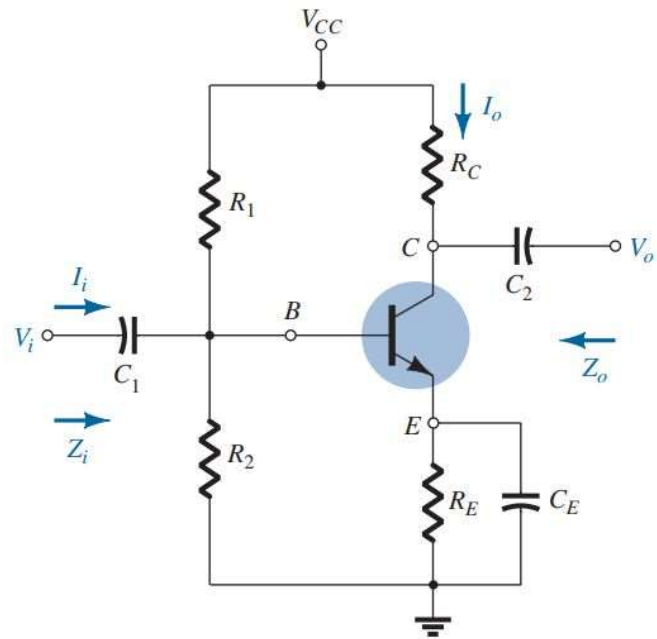

**FIG. 26**


Voltage-divider bias configuration.

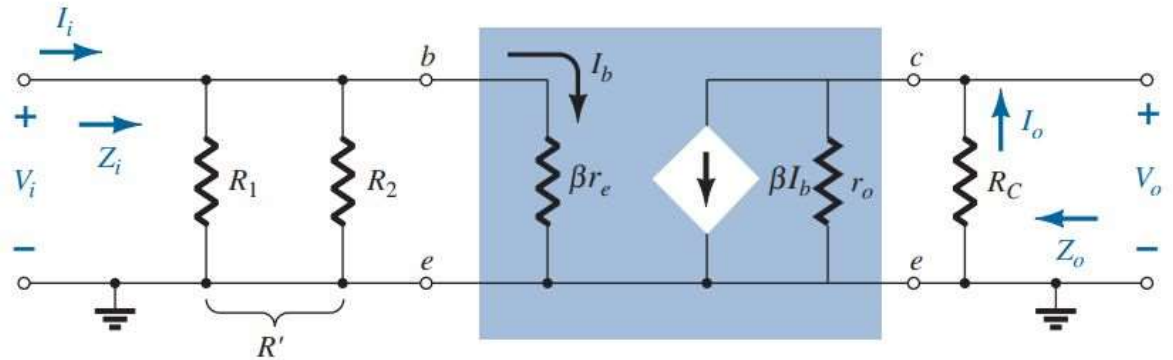

**FIG. 27**

Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 26.

## Voltage-divider Bias

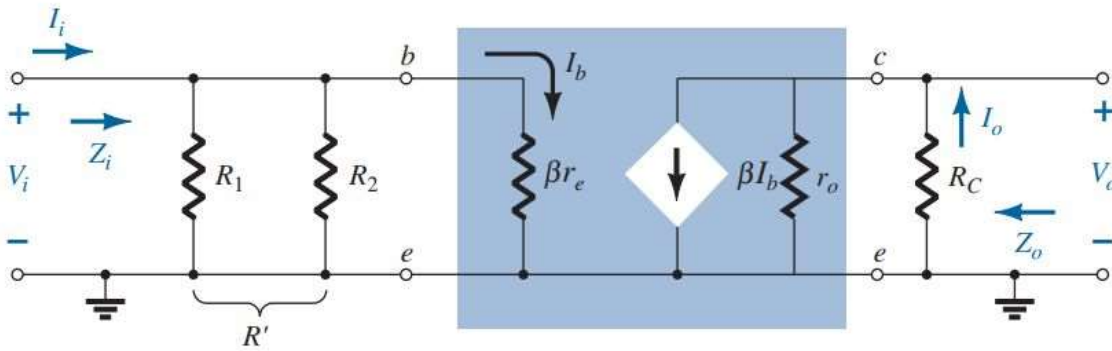


**FIG. 27**

*Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 26.*

## Voltage-divider Bias

**EXAMPLE 2** For the network of Fig. 28, determine:

- $r_e$ .
- $Z_i$ .
- $Z_o$  ( $r_o = \infty \Omega$ ).
- $A_v$  ( $r_o = \infty \Omega$ ).
- The parameters of parts (b) through (d) if  $r_o = 50 \text{ k}\Omega$  and compare results.

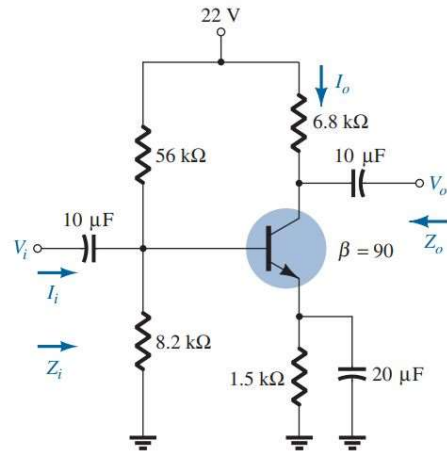

**FIG. 28**